

Name-Surname/SID: Jeren Annagurbanova/28517


## 1. Project Description

Designing a circuit that can both add and subtract two signed 20-bit integers and realize whether there is an overflow or not.

Design:

1. 20-bit ripple-carry adder-subtractor using full adders
  2. 20-bit hybrid adder-subtractor using five 5-bit carry lookahead adders (CLAs).
- Both adder-subtractors must detect overflow

## 2. First Design

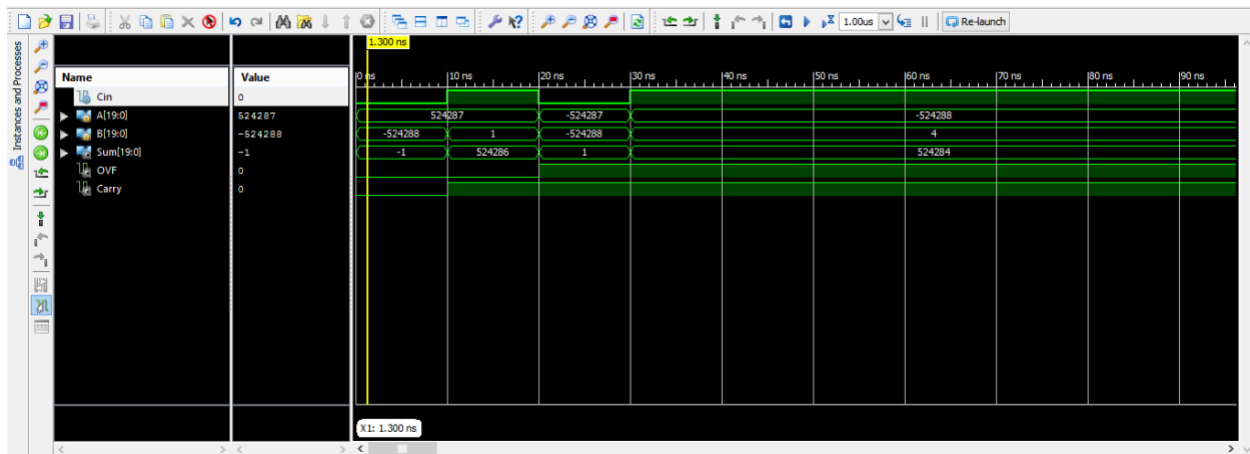

4 different test cases with addition and subtraction, both with and without overflow:


```
initial begin
    // Initialize Inputs
    // Addition with no overflow (524287) + (-524288) = should give -1
    A = (524287);
    B = (-524288);
    Cin = (0);
    #10;
    // subtraction with no overflow (524287) - 1 should give 524286
    A = (524287);
    B = (1);
    Cin = (1);
    #10;
    // Addition with overflow (-524287) + (-524288) should give overflow
    A = (-524287);
    B = (-524288);
    Cin = (0);
    #10;
    // Subtraction with Overflow (-524288) - (4) should give overflow
    A = (-524288);
    B = (4);
    Cin = (1);
    #10;
```

## Implementation Results Present implementation results

Area: # of LUTS 41 out of 1920

Time: 29.018ns

### 3. Second Design

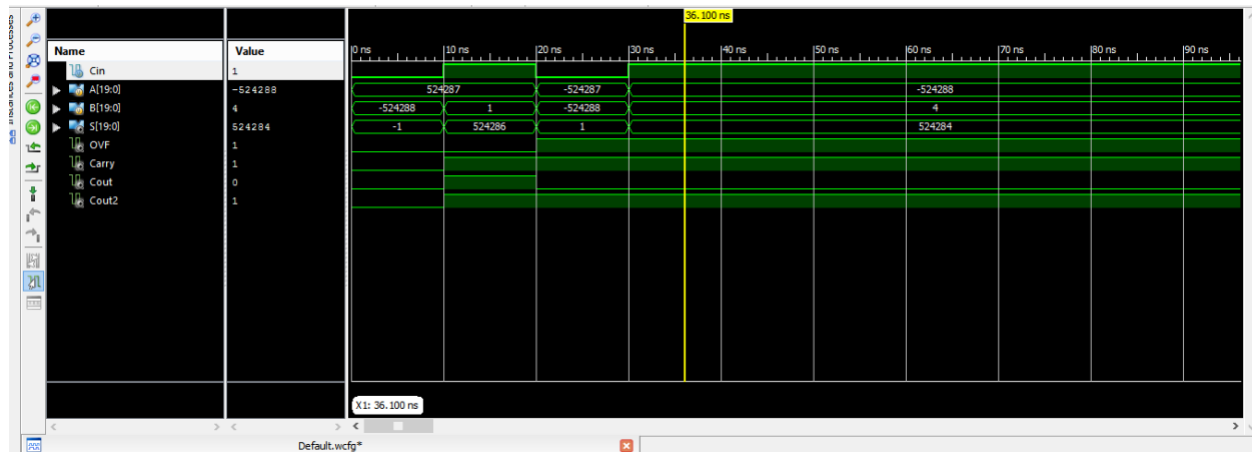

4 different test cases with addition and subtraction, both with and without overflow:

```
52 // Initialize Inputs
53 //Addition with no overflow (524287)+ (-524288) = should give -1
54 A = (524287);
55 B = (-524288);
56 Cin = (0);
57 #10;
58 //subtraction with no overflow (524287) - 1 should give 524286
59 A = (524287);
60 B = (1);
61 Cin = (1);
62 #10;
63 //Addition with overflow (-524287) + (-524288) should give overflow
64 A = (-524287);
65 B = (-524288);
66 Cin = (0);
67 #10;
68 //Subtraction with Overflow (-524288) - (4) should give overflow
69 A = (-524288);
70 B = (4);
71 Cin = (1);
72 #10;
73
```

## Implementation Results Present implementation results

Area: # of LUTS 48 out of 1920

Time: 28.042ns

#### 4. Questions

1) Ripple Carry:

Area: # of LUTS 41 out of 1920; Time: 29.018ns

Carry Lookahead:

Area: # of LUTS 48 out of 1920; Time: 28.042ns

Difference in terms of area:  $|48 - 41| = 7$

Difference in terms of time:  $|28.042 - 29.018| = 0.976 \text{ ns}$

2) Ripple carry adder/subtractor is better in terms of Area, its area is less than CL's area, ( $41 < 48$ )

3) CLA/S is better in terms of Time, it is faster than Ripple carry  
( $28.042\text{ns} < 29.018\text{ns}$ )

4) A new metric to measure the time-area tradeoff in two designs by multiplying the number of LUTs and time.

For RC:  $41 * 29.018\text{ns} = 1189.738$

For CL:  $48 * 28.042\text{ns} = 1346.016$

In this case, Ripple carry adder/subtractor is better according to the new metric